

# ECEN302 Lab 4 - Finite State Machines

Joshua Benfell - 300433229

August 30, 2020

## 1 Objectives

The primary objectives of this lab was to implement and understand different types of finite state machines. The machines that are being implemented here are the Mealy FSM and the Moore FSM. From doing this we will gain an understanding of the pros and cons of each type and where to use them.

## 2 Methodology

### 2.1 Introduction

In this lab a mealy and moore state machine will be implemented. The mealy state machine will be implemented as a mod three counter. The moore state machine will be designed such a particular 2 bit input will result in a predefined output. This will be done using the VHDL language.

### 2.2 Mealy FSM

A mod three counter was implemented as a mealy state machine. How this works is by inputting individual bits one at a time, if the current number of 1s seen is a multiple of 3, it will output high. The bit value is passed into the state machine on the rising edge of the clock cycle.

This was very difficult to think about as a mealy state machine due to there being so few states. A mealy state machine defines it's output based on the current state and the current input, however, there weren't enough states to make this an easy mealy state machine to think about.

The diagram for this FSM can be seen in Figure 1. The way this functions is that any input on states 1 and 2 output a 0. On state 1, if the input is a 0, the output is zero and if the input is a 1 the output is 1. This has the bug in that, due to the input not being passed through until the clock is done, the initial change to 1 causes an output of 1.

To verify the functionality a test bench was created to toggle the reset and input bits. The results of this testbench can be seen in Figure 2. From this we can see that aside from the aforementioned bug, the FSM functions as intended. 0 has been considered not a multiple of 3 as the example testbench results provided had the issue of it not making reset output a 0. So because of the inaccuracies, I opted to keep the reset as a 0 output, and ignore no input as a multiple of 3. The other discrepancy in the lab script is that the count of 6, if the input is 0, the output is 0. This is despite a count of 6 being a multiple of 3.

 


Figure 1: Mod 3 Mealy State Machine Diagram

So, this has been followed in this implementation, hence state 0 causing a 0 output on a 0 input.

 


Figure 2: Mod 3 Mealy State Machine Testbench Output

## 2.3 Moore FSM

The next type of FSM implemented is the moore state machine. On the input of 01 then 00, the output will become 0. On the input of 11 then 00, the output will become 1. On the input of 10 then 00, the output will toggle from it's current state. This state machine was implemented with 9 states, 1 for each case including when it was coming from a specific output route. The states are articulated in Figure 3 and it is laid out as TargetState : Input. This state machine is better implemented as a mealy state machine with the output fed back in as an input as it has events like toggling, which caused the biggest issue when thinking about how to implement this. Also, due to the fact that the input was a sequence of a pair and then 00, it caused issues in that the sequence could change before a 00, which meant that each state needed to be able to go between itself and a different sequence, which became even more complicated due to the toggle state. So to combat this, there is a route for if the output is 0 and if the output is 1. This solved all of the issues, but is much more complicated than if this were a mealy state machine. It is definitely possible to simplify this system, I couldn't think of a simpler way to do it though.

A testbench was created that provided the same input sequence as that provided in the lab script. This resulted in a similar simulation output to that provided in the lab script, shown in Figure 3. The major difference between this and the script image is the lack of a reset bit. This bit was not included because it wasn't really mentioned as an input into the system in the lab script as the primary input was the two bit sequence. So it was overlooked, and before I had noticed it was near the end of the session and I had already spent so long trying to get the state machines working in the first place.

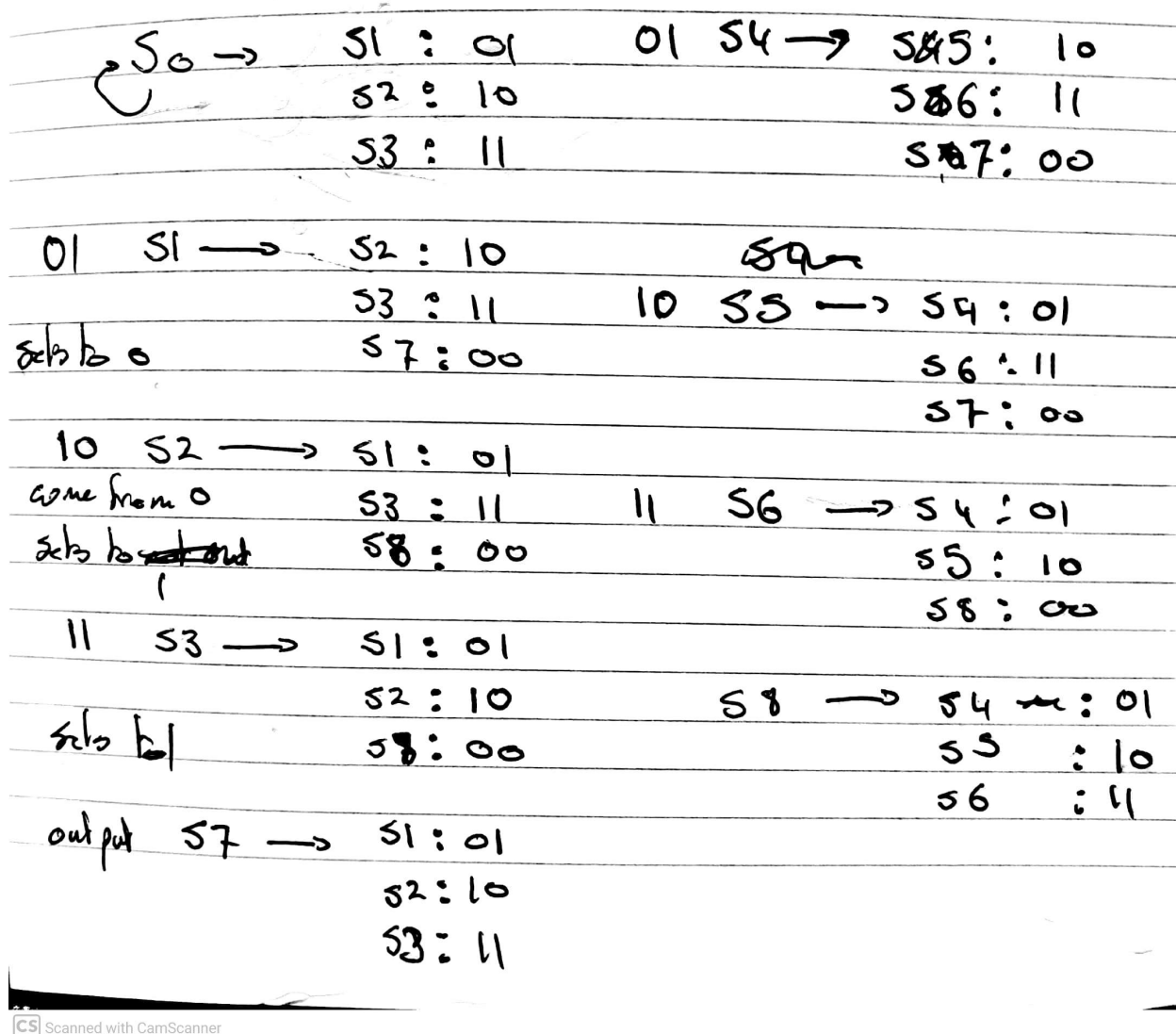


Figure 3: Moore State Machine Diagram

 


Figure 4: Moore State Machine Testbench Output

## 2.4 Code

### 2.4.1 Mealy State Machine

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use ieee.numeric_std.all;
4
5 entity Mealy_FSM_Mod_Three is
6     Port ( ain : in STD_LOGIC;
7           yout : out STD_LOGIC;
8           clk : in STD_LOGIC;
9           reset : in STD_LOGIC;
  
```

```

10         count : out STD_Logic_vector (3 downto 0) := "0000");
11 end Mealy_FSM_Mod_Three;
12
13 architecture Behavioral of Mealy_FSM_Mod_Three is
14
15 type state_type is (S0, S1, S2);
16 signal state, next_state : state_type; — Define signals for the states
17 signal counter : unsigned (3 downto 0) := "0000";
18
19 begin
20
21 SYNC_PROC : process (clk)
22 begin
23     if rising_edge(clk) then
24         if (reset = '1') then
25             state <= S0;
26             counter <= "0000";
27         else
28             state <= next_state;
29         end if;
30
31         if (ain = '1') then
32             counter <= counter + 1;
33         end if;
34     end if;
35 end process;
36
37 OUTPUT_DECODE : process(state, ain)
38 begin
39     case (state) is
40         when S0 =>
41             if (ain = '1') then
42                 yout <= '1';
43             else
44                 yout <= '0';
45             end if;
46         when others =>
47             yout <= '0';
48     end case;
49 end process;
50
51 NEXT_STATE_DECODE : process (state, ain)
52 begin
53     next_state <= S0;
54     case (state) is
55         when S0 =>
56             if (ain = '1') then
57                 next_state <= S1;
58             else
59                 next_state <= S0;
60             end if;
61         when S1 =>
62             if (ain = '1') then
63                 next_state <= S2;
64             else
65                 next_state <= S1;
66             end if;
67         when S2 =>
68             if (ain = '1') then

```

```

69         next_state <= S0;
70     else
71         next_state <= S2;
72     end if;
73 end case;
74 end process;
75
76 count <= std_logic_vector (counter);
77
78 end Behavioral;

```

code/Mealy\_FSM\_Mod\_Three.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Mealy_tb is
5  — Port ( );
6  end Mealy_tb;
7
8  architecture Behavioral of Mealy_tb is
9      component Mealy_FSM_Mod_Three
10         Port ( ain : in STD_LOGIC;
11              yout : out STD_LOGIC;
12              clk : in STD_LOGIC;
13              reset : in STD_LOGIC;
14              count : out std_logic_vector (3 downto 0)
15         );
16     end Component;
17
18     signal clk_int      : std_logic := '0';
19     signal ain_int      : STD_LOGIC := '0';
20     signal count_int     : std_logic_vector (3 downto 0) := "0000";
21     signal yout_int      : std_logic := '0';
22     signal reset_int     : std_logic := '0';
23 begin
24     uut: Mealy_FSM_Mod_Three port map (
25         ain => ain_int ,
26         yout => yout_int ,
27         clk => clk_int ,
28         reset => reset_int ,
29         count => count_int
30     );
31
32
33
34
35     process
36     begin
37         reset_int <= '1';
38         wait for 20ns;
39         reset_int <= '0';
40         wait for 20ns;
41         ain_int <= '1';
42         wait for 20ns;
43         ain_int <= '0';
44         wait for 60ns;
45         ain_int <= '1';
46         wait for 40ns;
47         ain_int <= '0';

```

```

48     wait for 40ns;
49 end process;
50
51 clk_int <= not clk_int after 5ns;
52 end Behavioral;

```

code/Mealy\_tb.vhd

## 2.4.2 Moore State Machine

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity MOOREFSM is
5      Port ( ain : in STD_LOGIC_VECTOR (1 downto 0);
6            yout : out STD_LOGIC;
7            clk : in STD_LOGIC);
8  end MOOREFSM;
9
10 architecture Behavioral of MOOREFSM is
11
12 type state_type is (S0, S1, S2, S3, S4, S5, S6, S7, S8);
13 signal state, next_state : state_type;
14 signal output : std_logic := '0';
15
16 begin
17
18     SYNC_PROC : process (clk)
19     begin
20         if rising_edge(clk) then
21             state <= next_state;
22         end if;
23     end process;
24
25     OUTPUT_DECODE : process (state)
26     begin
27         case (state) is
28             when S0 =>
29                 output <= '0';
30             when S7 =>
31                 output <= '0';
32             when S8 =>
33                 output <= '1';
34             when others =>
35                 output <= output;
36         end case;
37     end process;
38
39     yout <= output;
40
41     NEXT_STATE_DECODE : process (state, ain)
42     begin
43         next_state <= S0;
44         case (state) is
45             — State 0
46             when S0 =>
47                 if (ain = "01") then
48                     next_state <= S1;
49                 elsif (ain = "10") then
50                     next_state <= S2;

```

```

51         elsif (ain = "11") then
52             next_state <= S3;
53         else
54             next_state <= S0;
55         end if;
56 — State 1
57 when S1 =>
58     if (ain = "01") then
59         next_state <= S1;
60     elsif (ain = "10") then
61         next_state <= S2;
62     elsif (ain = "11") then
63         next_state <= S3;
64     else
65         next_state <= S7;
66     end if;
67 — State 2
68 when S2 =>
69     if (ain = "01") then
70         next_state <= S1;
71     elsif (ain = "10") then
72         next_state <= S2;
73     elsif (ain = "11") then
74         next_state <= S3;
75     else
76         next_state <= S8;
77     end if;
78 — State 3
79 when S3 =>
80     if (ain = "01") then
81         next_state <= S1;
82     elsif (ain = "10") then
83         next_state <= S2;
84     elsif (ain = "11") then
85         next_state <= S3;
86     else
87         next_state <= S8;
88     end if;
89 — State 4
90 when S4 =>
91     if (ain = "01") then
92         next_state <= S4;
93     elsif (ain = "10") then
94         next_state <= S5;
95     elsif (ain = "11") then
96         next_state <= S6;
97     else
98         next_state <= S7;
99     end if;
100 — State 5
101 when S5 =>
102     if (ain = "01") then
103         next_state <= S4;
104     elsif (ain = "10") then
105         next_state <= S5;
106     elsif (ain = "11") then
107         next_state <= S6;
108     else
109         next_state <= S7;

```

```

110         end if;
111     — State 6
112     when S6 =>
113         if (ain = "01") then
114             next_state <= S4;
115         elsif (ain = "10") then
116             next_state <= S5;
117         elsif (ain = "11") then
118             next_state <= S6;
119         else
120             next_state <= S8;
121         end if;
122     — State 7
123     when S7 =>
124         if (ain = "01") then
125             next_state <= S1;
126         elsif (ain = "10") then
127             next_state <= S2;
128         elsif (ain = "11") then
129             next_state <= S3;
130         else
131             next_state <= S7;
132         end if;
133     — State 8
134     when S8 =>
135         if (ain = "01") then
136             next_state <= S4;
137         elsif (ain = "10") then
138             next_state <= S5;
139         elsif (ain = "11") then
140             next_state <= S6;
141         else
142             next_state <= S8;
143         end if;
144     when others =>
145         next_state <= S0;
146     end case;
147 end process;
148
149 end Behavioral;

```

code/MOORE\_FSM.vhd

```

1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity MOORE_TB is
5 — Port ( );
6 end MOORE_TB;
7
8 architecture Behavioral of MOORE_TB is
9
10     component MOORE_FSM
11     Port ( ain : in STD_LOGIC_VECTOR (1 downto 0);
12           yout : out STD_LOGIC;
13           clk : in STD_LOGIC);
14     end component;
15
16     signal ain_int : std_logic_vector (1 downto 0) := "00";
17     signal yout_int : std_logic := '0';

```



```

18     signal clk_int    : std_logic := '0';
19
20 begin
21     uut: MOOREFSM PORT MAP (
22         ain => ain_int ,
23         yout => yout_int ,
24         clk => clk_int
25     );
26
27     clk_int <= not clk_int after 5ns;
28
29     process
30     begin
31         wait for 20ns;
32         ain_int <= "11";
33         wait for 10ns;
34         ain_int <= "10";
35         wait for 10ns;
36         ain_int <= "00";
37         wait for 20ns;
38         ain_int <= "10";
39         wait for 10ns;
40         ain_int <= "00";
41         wait for 10ns;
42         ain_int <= "11";
43         wait for 10ns;
44         ain_int <= "00";
45         wait for 10ns;
46         ain_int <= "01";
47         wait for 10ns;
48         ain_int <= "00";
49         wait for 10ns;
50         ain_int <= "10";
51         wait for 10ns;
52         ain_int <= "11";
53         wait for 10ns;
54         ain_int <= "00";
55         wait for 60ns;
56
57     end process;
58
59 end Behavioral;

```

code/MOORE\_TB.vhd